

EEE232 Project

A 3-Stage 5W Audio Amplifier


Onat FİLİK 20200607020

Ünal Karadayı 20200607027

Electrical & Electronics Engineering



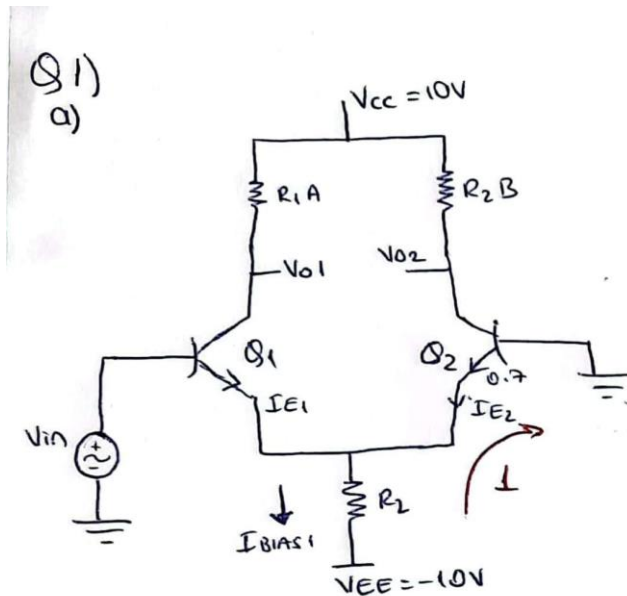Q1. Determine values for the resistances R_{1A} , R_{1B} , and R_2 to achieve the following bias voltages and currents (assume $\beta = 100$ for each transistor). (Hints: Apply superposition and symmetry).



$$I_{E1} + I_{E2} = 500 \mu A$$

$$I_{E1} = I_{E2}$$

$$I_{E1} = I_{E2} = \frac{500}{2} \mu A = 250 \mu A$$

$$V_{01} = 10 - R_{1A} I_{E1}$$

$$9.3 = 10 - R_{1A} (250 \mu A)$$

$$R_{1A} = 2.8 \text{ k}\Omega$$

$$V_{02} = 10 - R_{1B} I_{E2}$$

$$9.3 = 10 - R_{1B} (250 \mu A)$$


$$R_{1B} = 2.8 \text{ k}\Omega$$

KVL at 1

$$-10 + R_2 (500 \mu A) + 0.7 = 0$$

$$R_2 = 18.6 \text{ k}\Omega$$

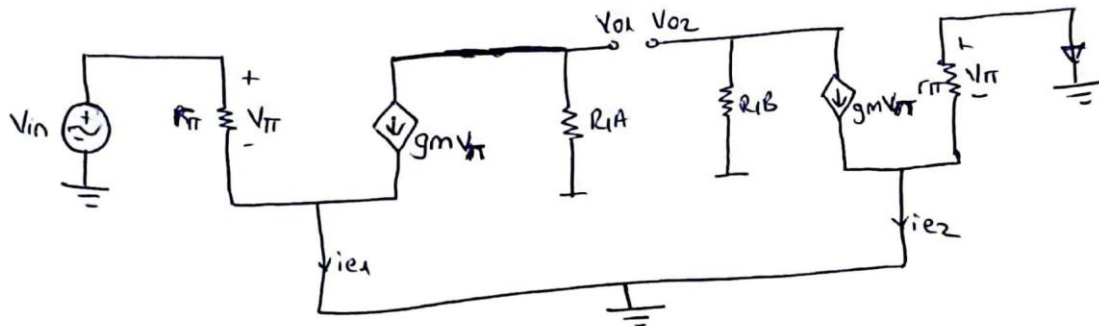Q2. Now, by performing small-signal analysis find the following: i. Small-signal voltage gains V_{O1}/V_{in} and V_{O2}/V_{in} . ii. Differential output gain $(V_{O1}-V_{O2})/V_{in}$. iii. Small-signal input resistance R_{in} at the input to the amplifier.



$$I_{BIAS} = 500 \mu A$$

$$V_T = 26 mV$$

$$i_{e1} = i_{e2} = 250 \mu A = \frac{I_{BIAS}}{2}$$

$$I_B = \frac{2.5 \times 10^{-4}}{100} = \frac{i_{e1}}{\beta}$$

$$I_B = 2.5 \times 10^{-6} A$$

$$r_{\pi} = \frac{V_T}{I_B} = \frac{26 mV}{2.5 \times 10^{-6}} = 10.4 k\Omega$$

$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{10.4}$$

$$g_m = 9.62 \times 10^{-3} S$$

$$V_{O1} = -R_A \cdot g_m \cdot V_{\pi}$$

$$\frac{V_{O1}}{V_{in}} = -R_A \cdot g_m$$

$$= -26.9$$

$$V_{O2} = -R_B \cdot g_m \cdot V_{\pi}$$


$$\frac{V_{O2}}{V_{in}} = -R_B \cdot g_m$$

$$= -26.9$$


$$\frac{V_{O1} - V_{O2}}{V_{in}} = 0$$

$$R_{in} = 2r_{\pi} = 20.8 k\Omega$$

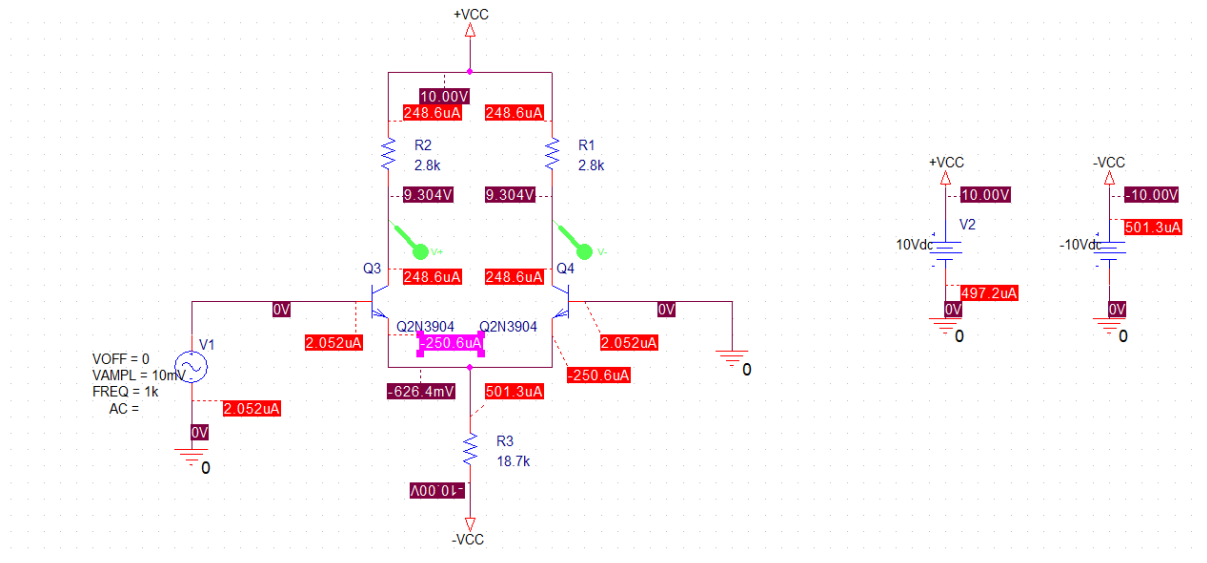
Q3. Produce graphs of $V_{O1}(t)$, $V_{O2}(t)$ and $V_{O1}(t) - V_{O2}(t)$ for an input signal of V_{in} being a 10mVpk 1kHz sine wave signal.




V_{O1} :

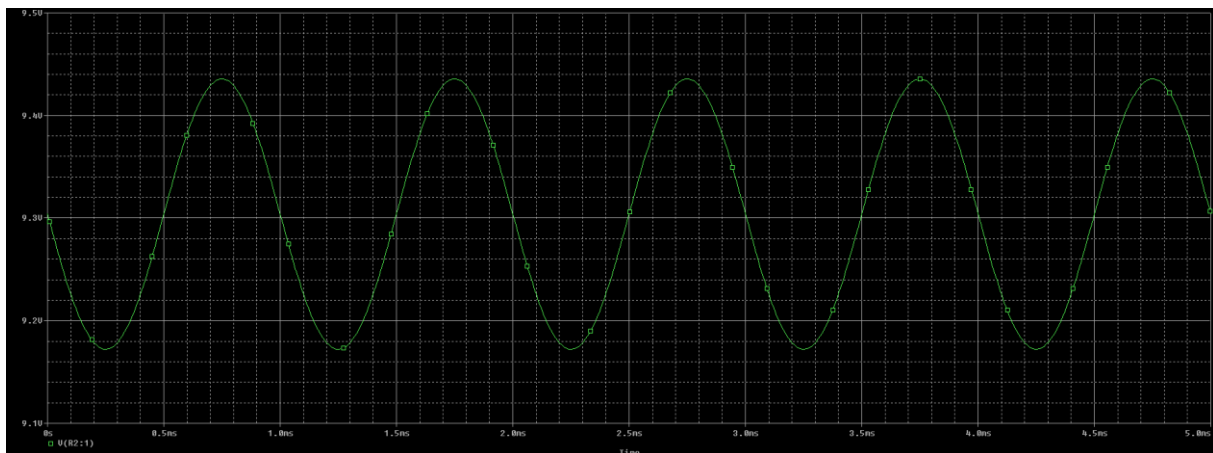


V_{O2} :

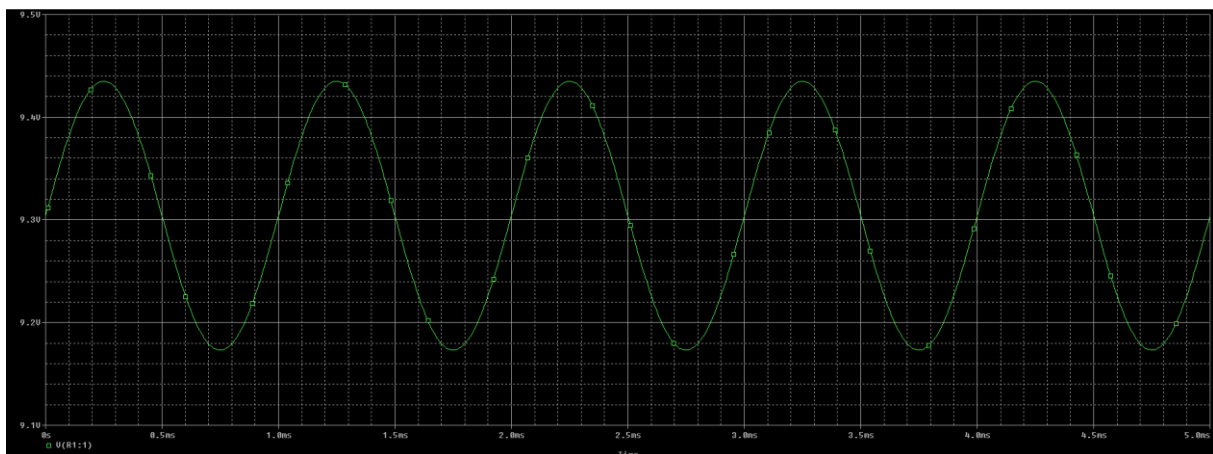

V01 (Red) and V02 (Green):

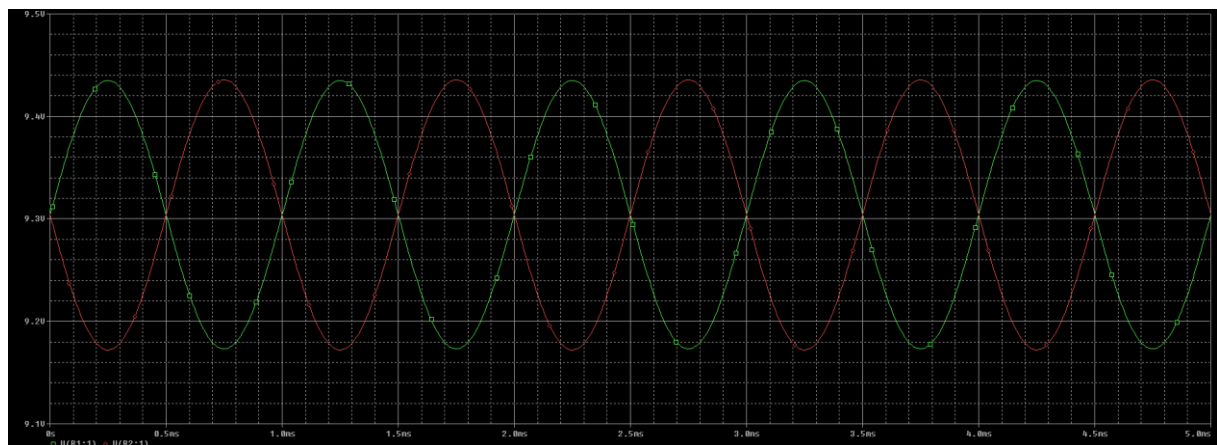


V01-V02:

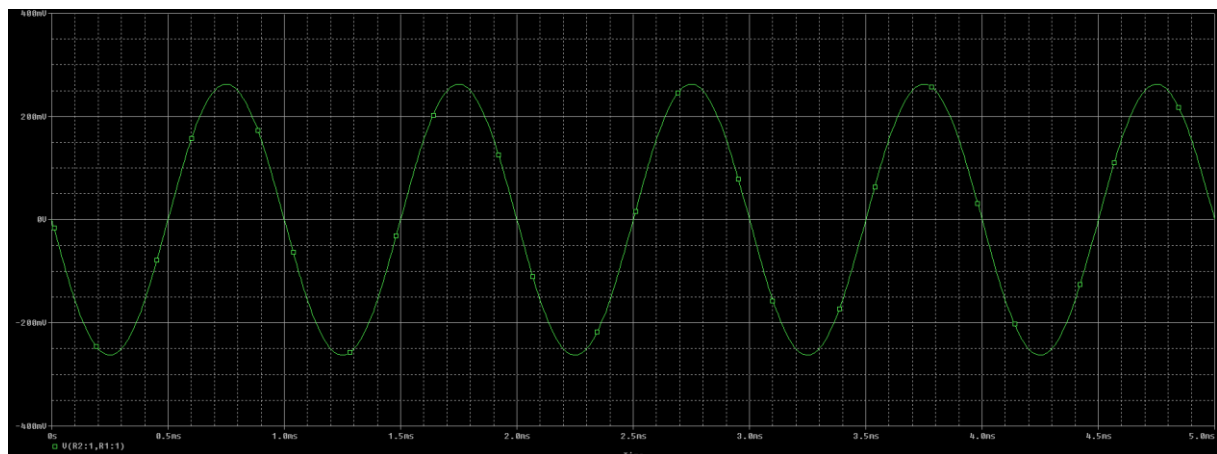

Q4. The actual current source circuit is comprised of a NPN BJT and a voltage divider network (oval insert). Choose values for the resistors R_3 , R_4 and R_5 to achieve the following specifications (assuming $\beta = 100$):

Stage 2

Q4)

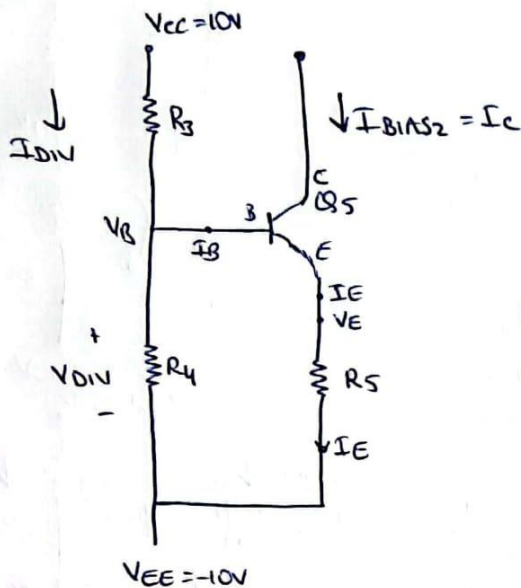

$$I_{BIAS2} = 20\text{mA}$$

$$I_{DIV} = 1.8\text{mA}$$

$$V_{DIV} = 1.7V$$

$$V_{CC} = 10V$$

$$V_{EE} = -10V$$

$$\beta = 100$$

Given that $\beta = 100$ a huge number. Hence I_B is insignificant

$$I_C \approx I_E$$

$$I_{BIAS2} = I_C$$

$$I_C \approx 20\text{mA}$$

$$\text{SO, } I_E \approx 20\text{mA}$$

$$V_B = V_{DIV} + V_{EE}$$

$$= 1.7 - 10V$$

$$= -8.3V$$

$$I_{DIV} = \frac{V_{CC} - V_B}{R_3} = \frac{10 - (-8.3)}{R_3}$$

$$R_3 = \frac{10 - (-8.3)}{1.8} = 10.2\text{ k}\Omega$$

$$R_3 = 10.2\text{ k}\Omega //$$

$$R_4 = \frac{V_{DIV}}{I_{DIV}} = \frac{1.7}{1.8} = 0.9\text{ k}\Omega$$

$$R_4 = 0.9\text{ k}\Omega //$$

$$R_3 + R_4 = \frac{V_{CC} + V_{EE}}{I_{DIV}} = \frac{20}{1.8} = 11.1 //$$

$$10.2 + 0.9 = 11.1 //$$

Applying KVL at loop 1

$$-1.7 + V_{BE} + I_{BIAS2} \cdot R_5 = 0$$

$$-1.7 + 0.7 + I_{BIAS2} \cdot R_5 = 0$$

$$\overset{20\mu A}{I_{BIAS2}} \cdot R_5 = 1.00$$

$$R_5 = \frac{1}{20\mu A} = \frac{1}{20 \times 10^{-3}} = 50\Omega$$

$$R_5 = 50\Omega$$

$$I_B = \frac{I_C}{\beta} = \frac{20}{100} = 0.2\mu A //$$


$$I_{DIV} = I_B + I_{R_4}$$

$$1.8 = 0.2 + I_{R_4}$$


$$I_{R_4} = 1.6 //$$

Q5. Using DC ANALYSIS in simulation, verify the values of I_{BIAS2} , I_{DIV} and V_{DIV} . Connect the output of the current source to a separate DC supply (V_S) and use DC SWEEP analysis to vary the voltage from -10 to +10 Volts. Produce a plot of I_{BIAS2} as a function of V_S . What is the dynamic voltage range of the output?

Sketch:


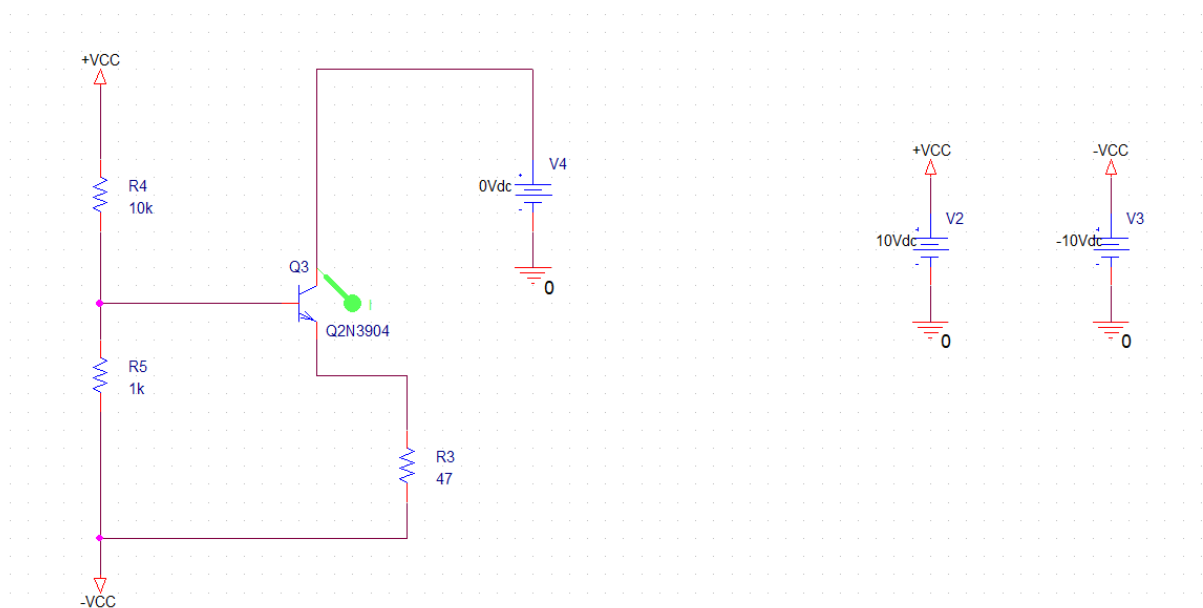


Simulation:

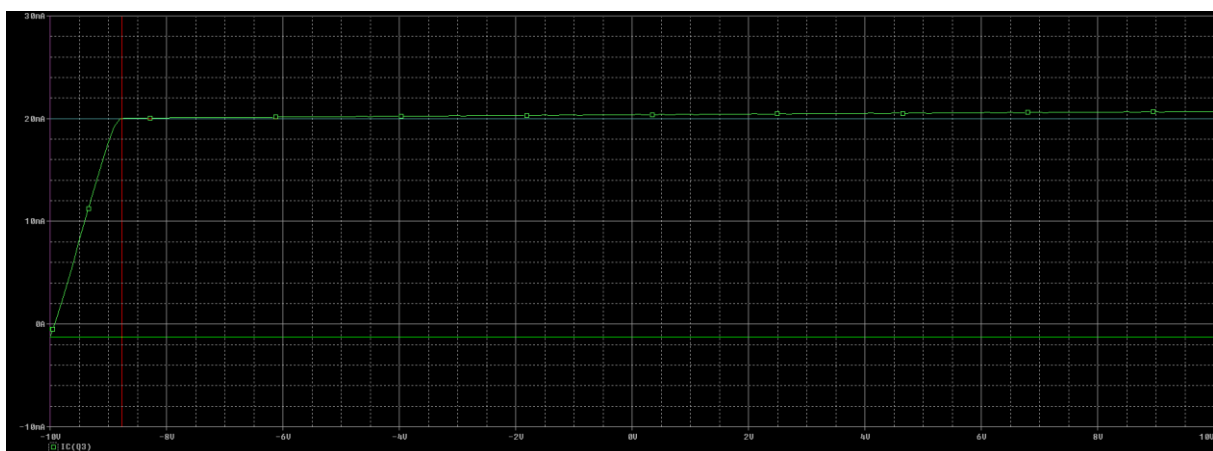

Q6. What is the maximum voltage that this circuit can deliver to the load? What percentage of the signal is this value?

Q6-

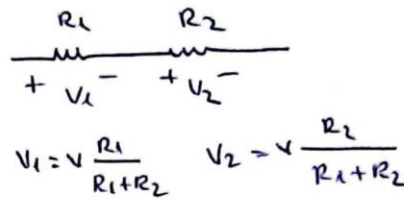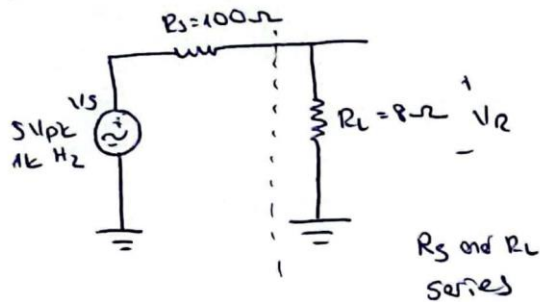

The voltage across the load R_L using the voltage division rule

$$V_R = V_{pk} \frac{R_L}{R_s + R_L}$$

$$5 \cdot \frac{8}{108} = 0.370$$


The circuit's maximum voltage delivery to a load is $V_R = 0.37V$

$R_s + R_L \rightarrow \text{minimum}$

$\frac{V_s}{R_s + R_L} \rightarrow \text{maximum}$

Q7. Using the small-signal model for this amplifier, determine the effective output impedance R_{out} of this stage (assume $\beta = 50$ for the power transistor Q4).

Stage 3

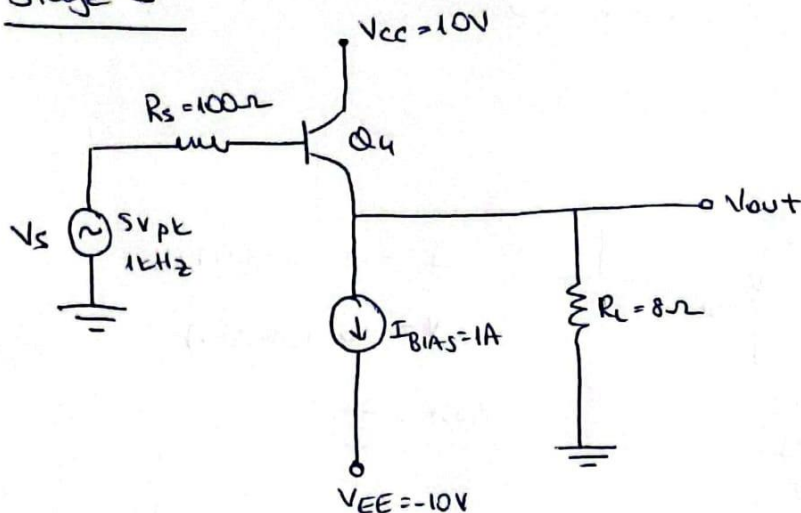

$$I_E = 1A \quad \beta = 50$$

$$I_C = \left(\frac{\beta}{\beta + 1} \right) I_E = \left(\frac{50}{50 + 1} \right) \times 1$$



$$I_C = 0.980A$$

$$\text{Transconductance} \quad g_m = \frac{I_C}{V_T}$$

$$V_T = 26mV$$

$$g_m = \frac{0.980}{0.026} = 37.7 A/V$$
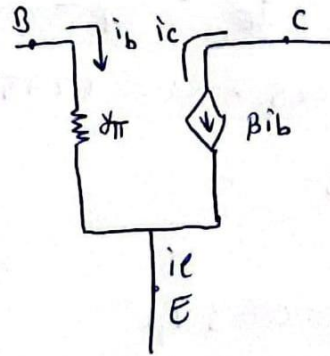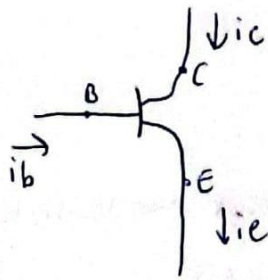
$$r_{\pi} = \frac{\beta}{g_m} = \frac{50}{37.7} = 1.326$$




$$\begin{aligned} i_e &= i_b + i_c \\ i_e &= i_b + \beta i_b \\ i_e &= (\beta + 1) i_b \end{aligned}$$

Turn off all of the DC source
Transistor should be replaced with AC
comparable model, $V_s = 0V$

CS CamScanner ile tarandı

$$R_{out} = \left(\frac{V}{I} \right) \Omega \quad \text{This is output resistance without load}$$

$$R'_{out} = R_{out} \parallel R_L$$

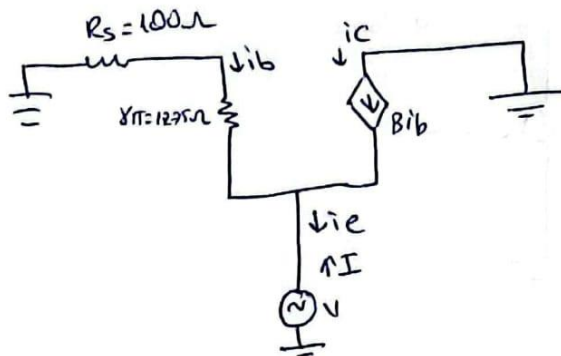

$$I = -i_e = -(\beta + 1) i_b$$

$$V = -i_b (r_{\pi} + R_s)$$

$$R_{out} = \frac{V}{I}$$

$$= \frac{-i_b (r_{\pi} + R_s)}{-i_b (\beta + 1)}$$

$$= \frac{r_{\pi} + R_s}{\beta + 1} = \frac{1.326 + 100}{50 + 1}$$

$$R_{out} = 1.987 \Omega$$

$$\begin{aligned} R'_{out} &= (R_{out} \parallel R_L) \\ &= \frac{(1.987) \cdot (8)}{(1.987 + 8)} \end{aligned}$$

$$R'_{out} = 1.59 \Omega \quad \text{This is output resistance with load}$$

Q8. What is the peak voltage delivered to the load using the Emitter Follower.

Q9. How does this output compare to the circuit without the transistor?

$$8) V_s = 5V_p \quad R_e = \frac{V_T}{I_E} = \frac{0.026}{1} = 0.026$$

$$R_{\pi} = R_e (\beta + 1) = 0.026 \times 51 = 1.326 \Omega$$

$$V_{out} = \frac{R_{\pi}}{R_s + R_{\pi}} \times V_s$$


$$\frac{1.326 \times 5}{100 + 1.326} = 0.065V_p$$

9) without the transistor


$$V_{out} = \frac{8 \times 5}{100 + 8} = 0.370$$

Q10. Using TRANSIENT ANALYSIS, verify these results in simulation.

Sketch:

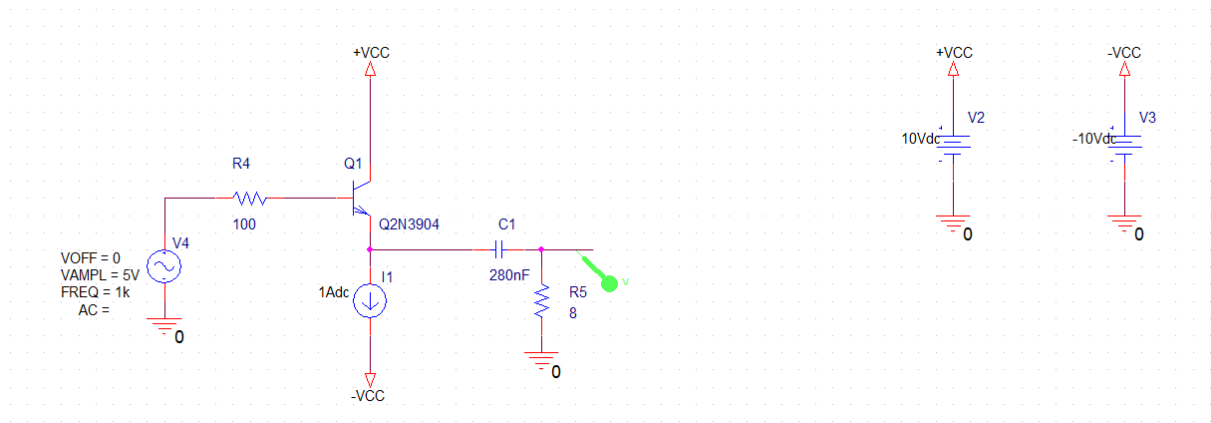

Simulation:

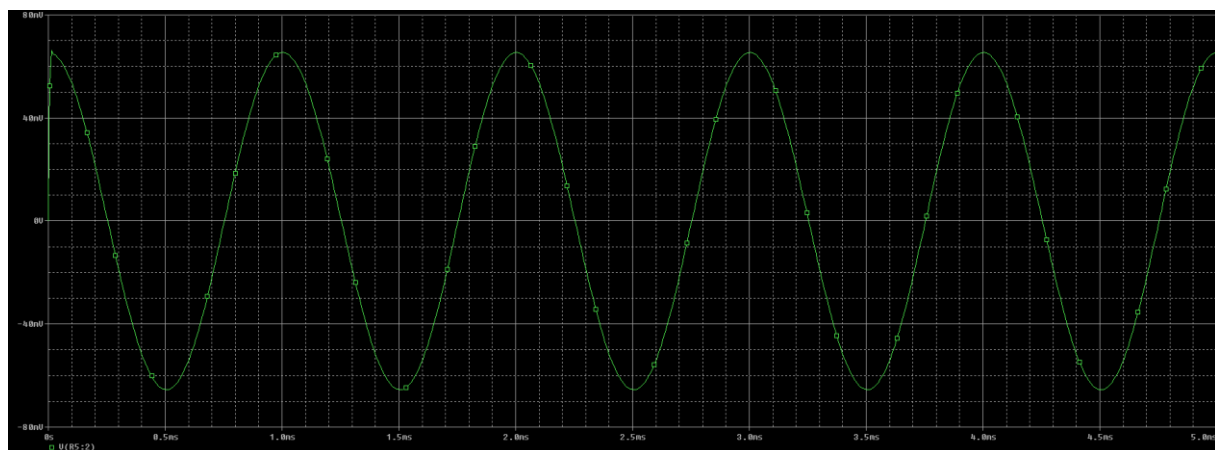

Q11. Measure the DC Bias values before injecting the input signal and include them in your report.

IBIAS1:



IBIAS2:




IBIAS3:



Q12. Test the amplifier with a real input signal (mp3 player, iPod, guitar pick-up, etc.), and demonstrate the working audio amplifier circuit to your TA.

Breadboard:

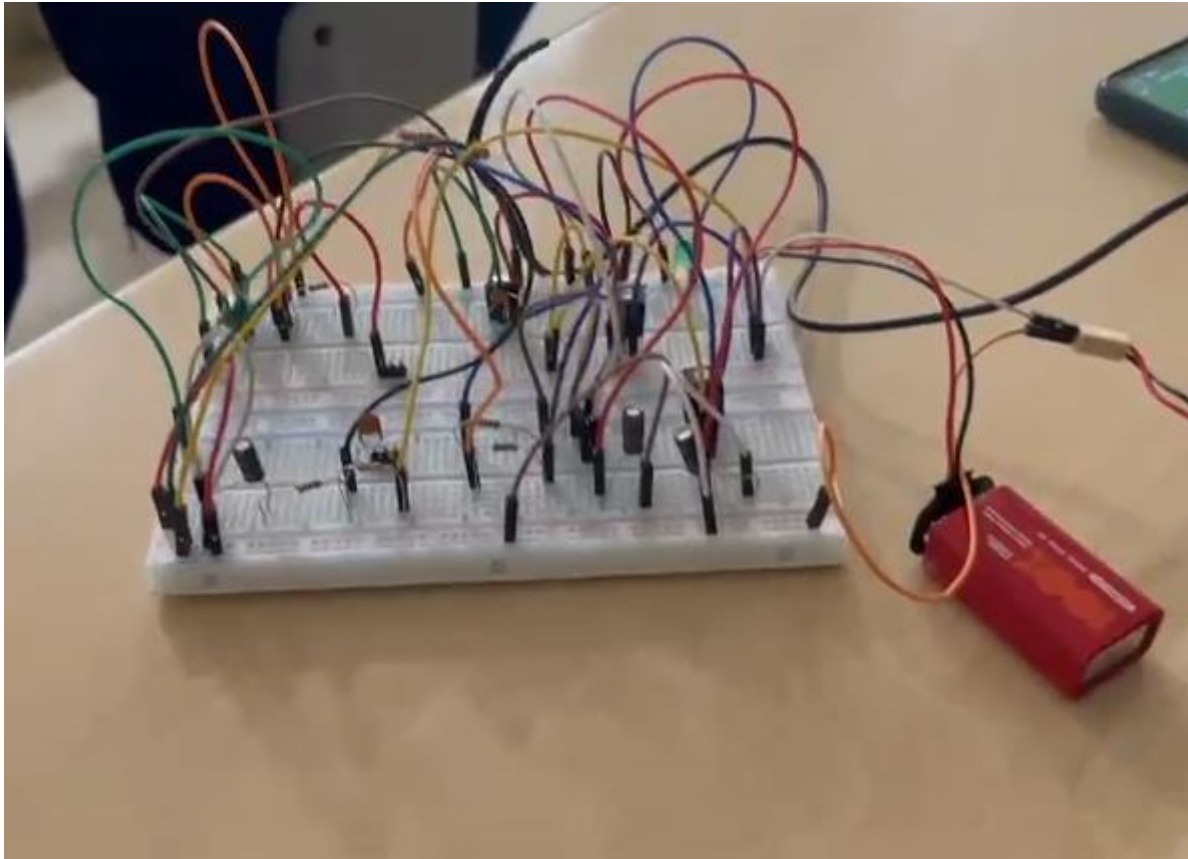


Test Video:




232ONATUNAL.mp4


Sketch:

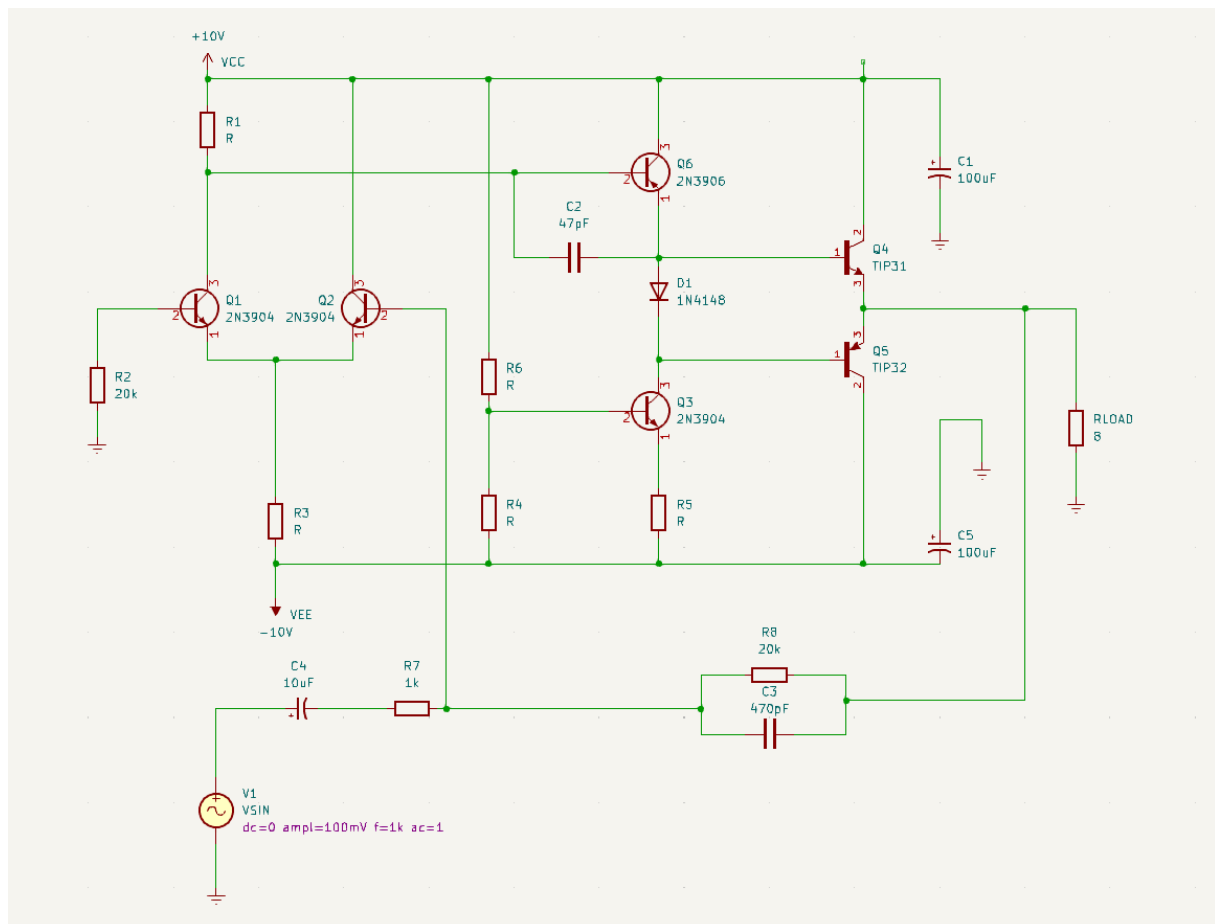

PCB:

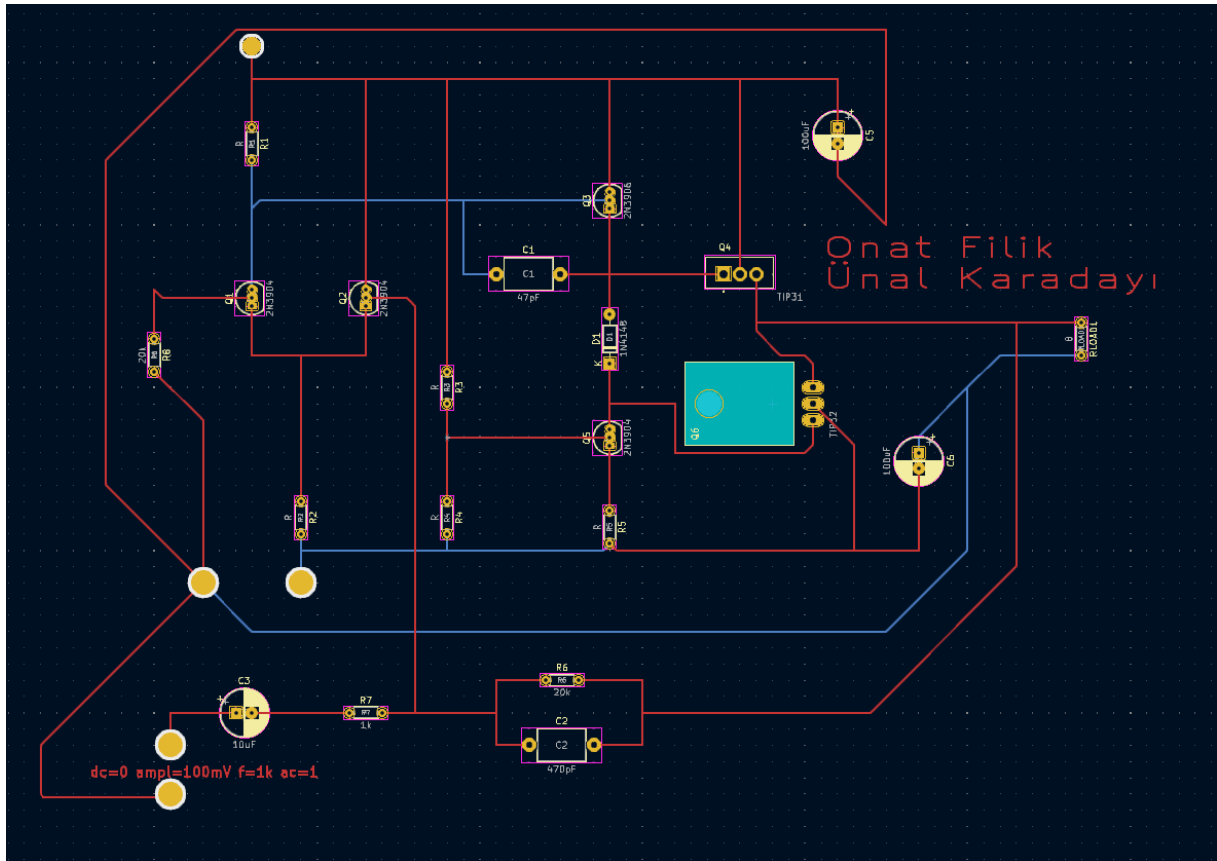

PCB 3D Front:

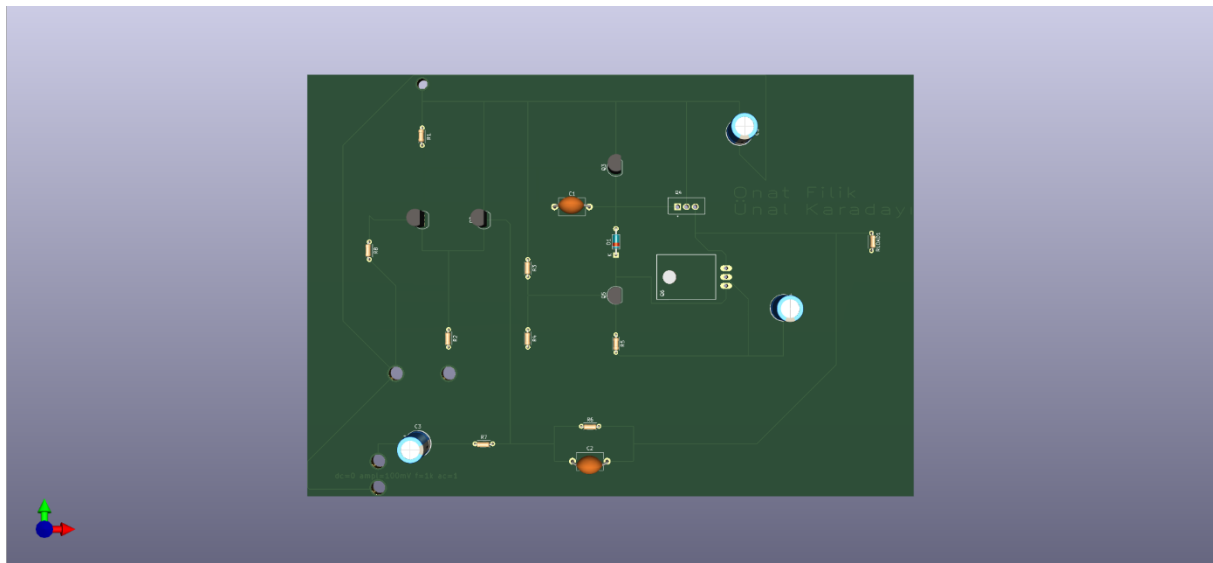

PCB 3D Rear:

